

Section IV: Electrical

1. What is the equation for Ohm's law?

- A. $V = IR$ B. $V = I/R$ C. $R = VI$ D. $I = VR$


2. In direct current $I = 3A$ $R = 4\Omega$ Calculate V

- A. 1.33 V B. 6 V C. 12 V D. 24 V

3. What becomes V if we use 2 resistors of 4Ω in parallel?


- A. 2.66 V B. 6 V C. 12 V D. 24 V

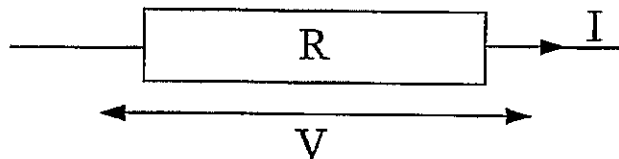4. If the resistor below is 100 ohms and the voltage drop is 220 volts, what is the current I ?




- A. .22 A B. 22 A C. 2.2 A D. 2.0 A

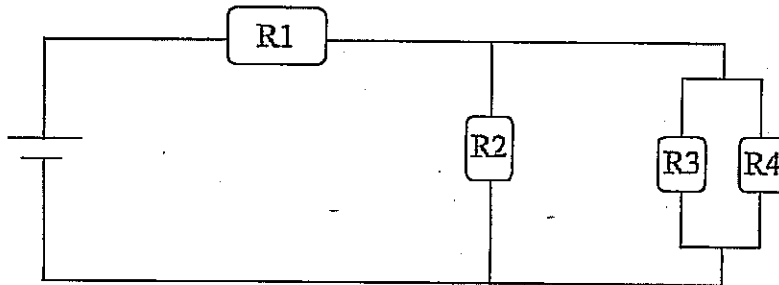5. If $R1 = 2k$ ohms, $R2 = 1k$ ohms, $R3 = 2k$ ohms and $R4 = 2k$ ohms, what is the equivalent resistance of the circuit?




- A. 2250 ohms B. 1500 ohms C. 2500 ohms D. 2000 ohms

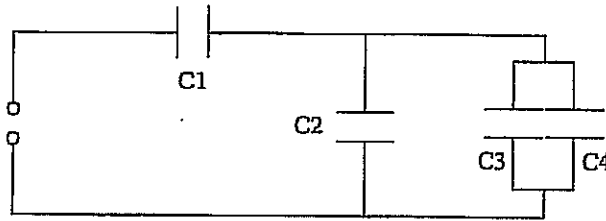6. If $C_1=6F$, $C_2=1F$, $C_3=1F$ and $C_4=1F$, what is the equivalent capacitance of the circuit shown below?



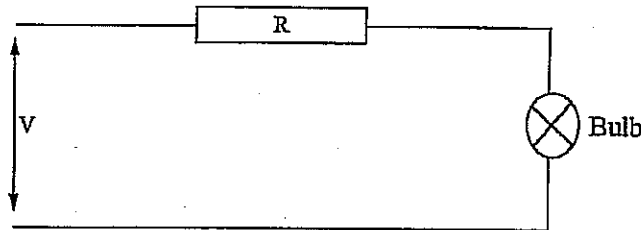- A. 2F B. 1.75 F C. 2.25 F D. 2.125 F
7. To reverse the direction of rotation in a 3hp, AC motor we must:
- A. Change round all three wires cyclically.
 B. Change round any two wires
 C. Cannot change direction of rotation.
 D. Change switch position, ie "on" de-energized and "off" energized to get the reversed direction.
8. For the circuit shown below, if $V=380VAC$ and the bulb is rated at $170VAC$, $5W$, what is the resistance R that should be connected in series to the bulb?




- A. 6500 ohms B. 7000 ohms C. 7145 ohms D. 5780 ohms
9. If we increase the voltage across a DC motor, then the motor speed will?
- A. decrease B. increase C. stay same D. stop
10. What will be the output voltage of two 12V batteries connected in series?
- A. 12 V B. 6 V C. 24 V D. no voltage

11. What will be the output voltage of two 12V batteries connected in parallel?

- A. 12 V B. 6 V C. 24 V D. no voltage

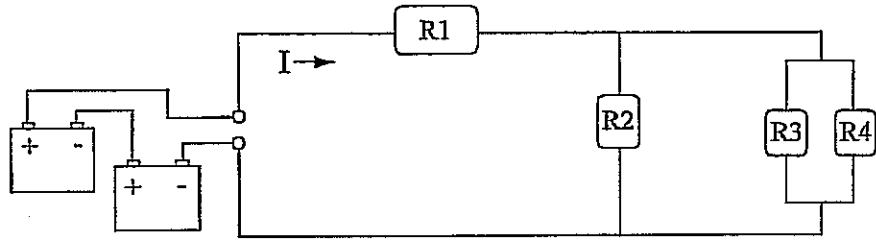12. In the circuit shown below what is the current if the batteries are 12V each, $R_1=20$ ohms, $R_2=10$ ohms, $R_3=20$ ohms, and $R_4=20$ ohms?



- A. 1000 mA B. 660 mA C. 960 mA D. 1200 mA